

Lamp Current Threshold Detection Circuit (0.11A Monitoring System)

This project is a transistor-based current threshold detection circuit designed to verify whether a 12V lamp is operating within its specified current consumption of 0.11A.

The system monitors the lamp current and provides a clear visual indication using two LEDs:

- Green LED ON → Lamp current is 0.11A or higher (Normal operation)
- Red LED ON → Lamp current is below 0.11A (Fault or underperformance)

How It Works

- A sensing resistor network converts lamp current into a proportional voltage.
- Q1 (2N2222A) acts as the main current-sensing transistor.
- When the sensed current reaches the calibrated threshold (~0.11A), Q1 switches state.
- A transistor switching stage (Q2 and Q3) forms a signal inverter/driver stage.
- Depending on the detected current level:
 - One transistor path activates the green LED
 - The opposite path activates the red LED
- A 9V supply powers the control circuit.

Use cases:

Lamp production testing

Load verification systems

Automotive bulb diagnostics





